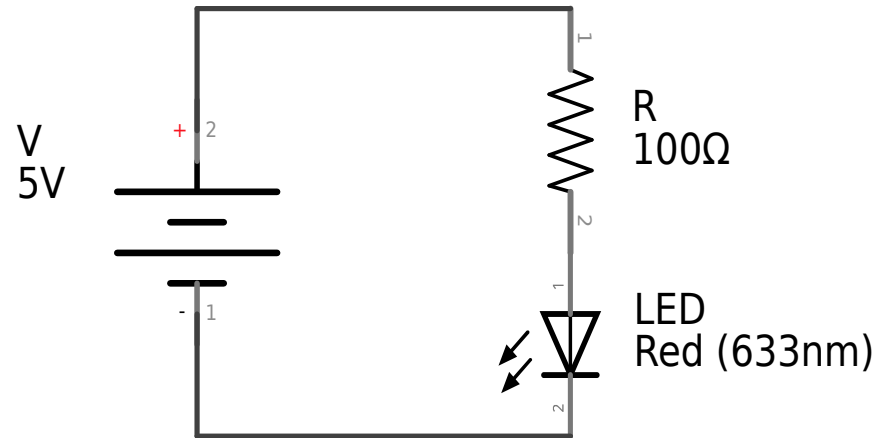


# *12 Ways to Blink an LED*



Charlotte Hackerspace  
Neil Roeth

# LED basic circuit





- Need to limit current (no magic smoke)
- $V = V_{\text{LED}} + V_{\text{R}}$
- $V_{\text{R}} = IR$  (Ohm's Law)
- $V = V_{\text{LED}} + IR \Rightarrow R = (V - V_{\text{LED}})/I$
- LED:  $V_{\text{LED}} \sim 2.5\text{V}$
- Raspberry Pi: 3.3V, 16mA
- $R = (3.3 - 2.5)/0.016 = 50 \text{ ohms}$
- Arduino: 5V, 40mA
- $R = (5 - 2.5)/0.040 = 62.5 \text{ ohms}$
- Bigger is safer

# Blink LED with pushbutton

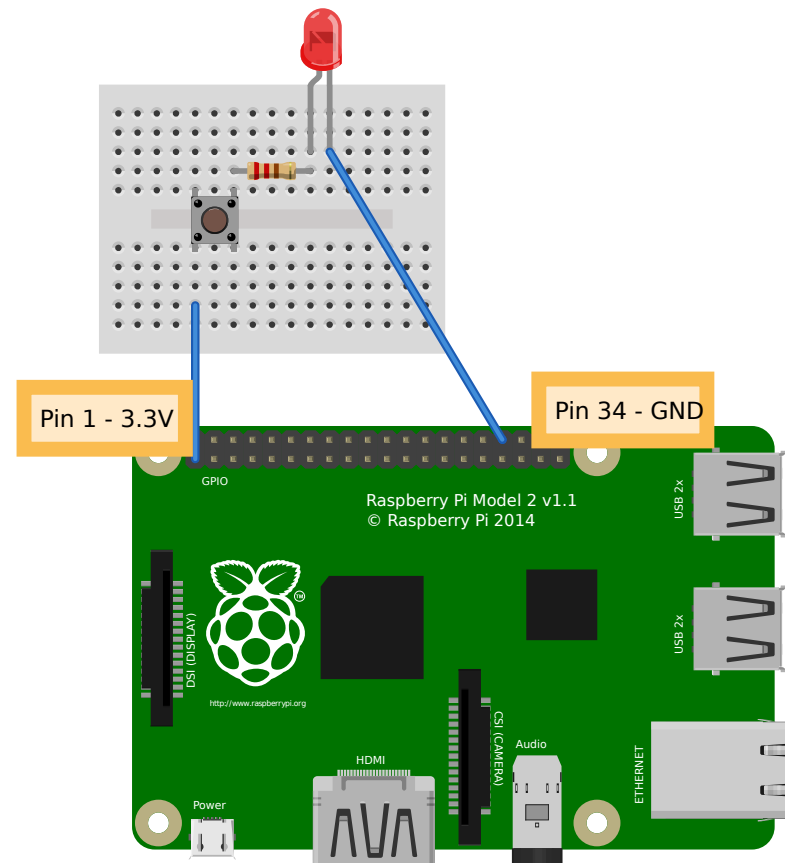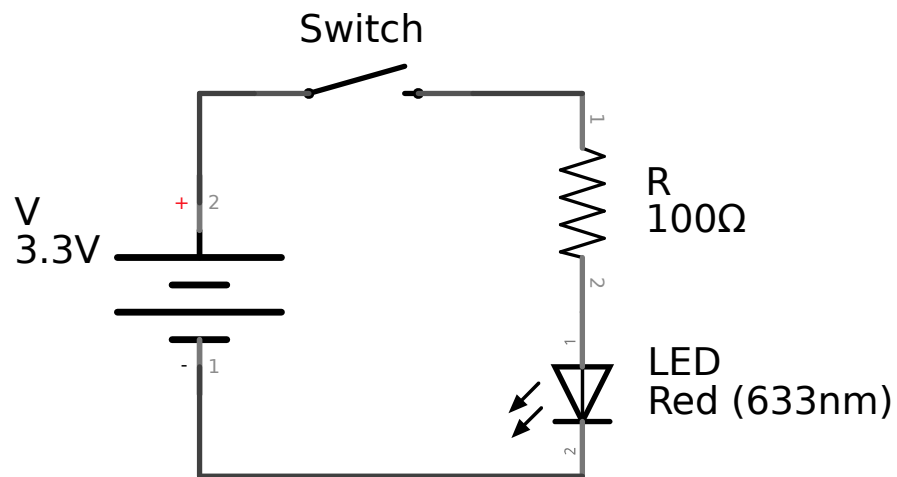

# Blink LED with Pi

Raspberry Pi1

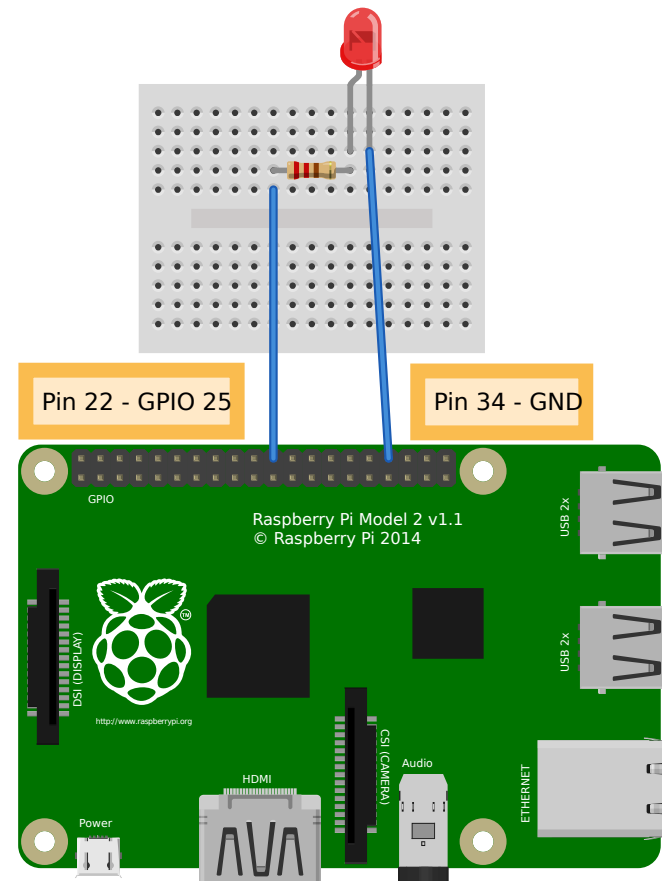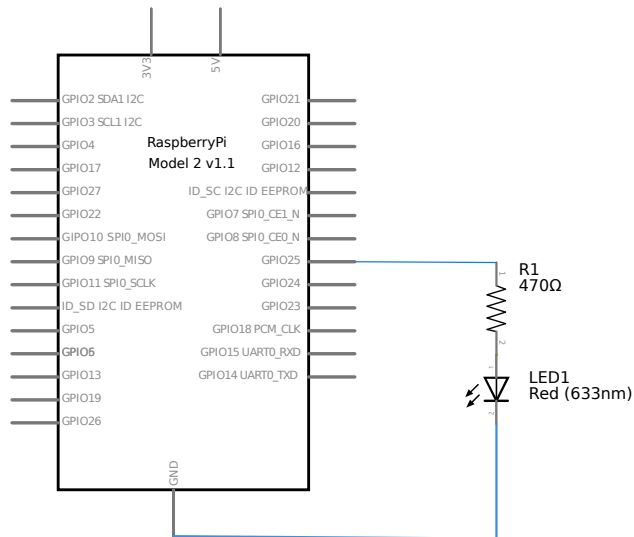

- Create a file named BlinkRaspberryPi.py with Python code:

```
import RPi.GPIO as GPIO
import time
```

```
GPIO.setmode(GPIO.BCM)
GPIO.setup(25, GPIO.OUT)
```



```
while True:
    GPIO.output(25, GPIO.HIGH)
    time.sleep(1)
    GPIO.output(25, GPIO.LOW)
    time.sleep(1)
```

- Ensure you have the Python libraries for accessing GPIO pins installed:

```
$ sudo apt-get install python-rpi.gpio python3-rpi.gpio
```


- Run it: `python BlinkRaspberryPi.py`
- What does script do?
- Raspberry Pi has digital outputs only (HIGH, LOW)

# 555 Astable Multivibrator

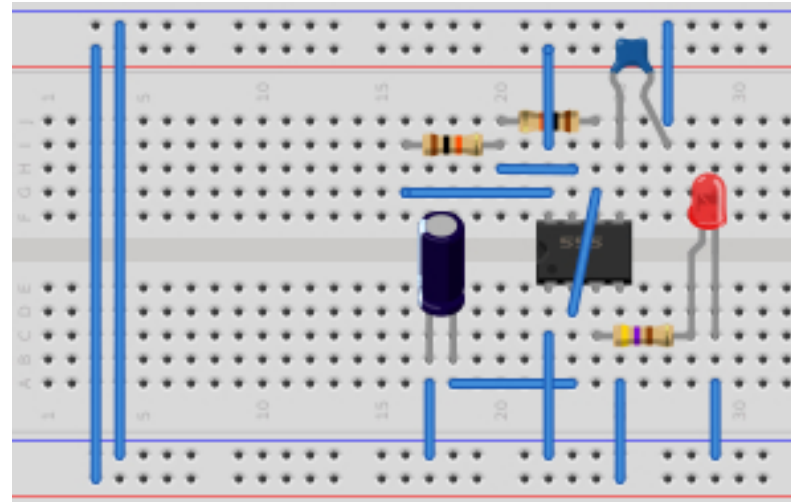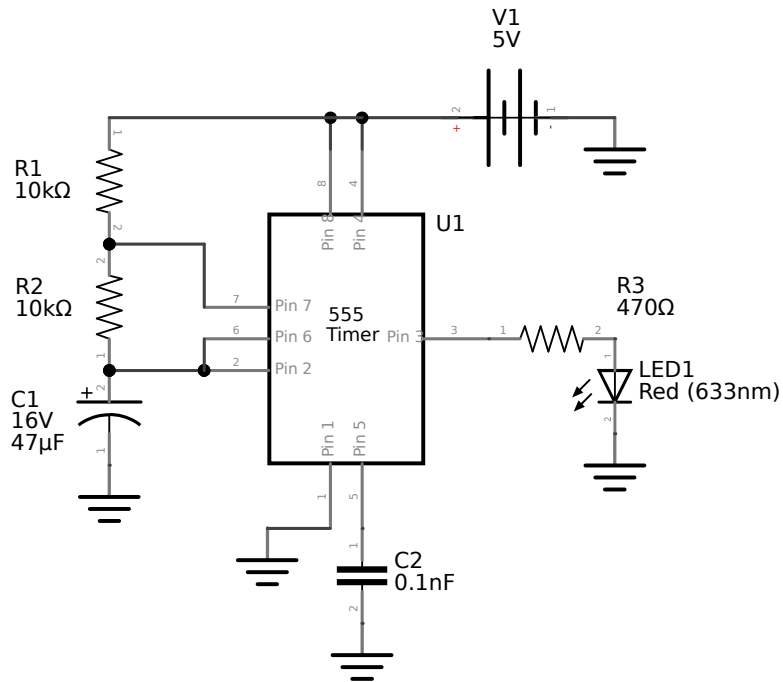


- Connect 5V from Pi to red rail, ground to blue rail
- Dot on IC is pin 1, C1 has +/-
- Timing is determined by how quickly capacitor C1 charges/discharges

# How the 555 circuit works

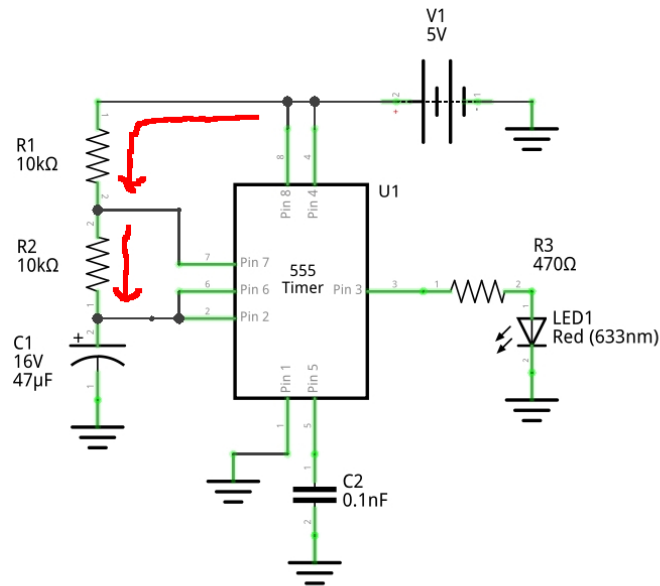

fritzing

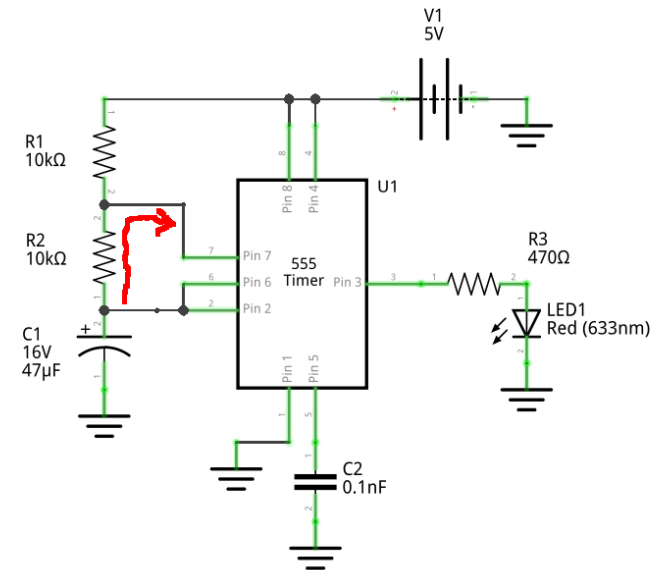

fritzing

- Charging (left): Capacitor C1 charges through R1 and R2
- When capacitor voltage reaches  $\frac{2}{3} V_1$ , pin 7 connects to ground
- Discharging (right): Capacitor C1 discharges through R2
- When capacitor drops to  $\frac{1}{3} V_1$ , pin 7 disconnects from ground
- Water analogy: voltage like pressure, current like flow rate
- Capacitor like bucket, resistor like hose restriction
- Bigger capacitor or bigger resistor means longer time
- Time constant for charging =  $(R1+R2)*C1$
- Time constant for discharging =  $R2*C1$

# Arduino

- <https://www.arduino.cc/> , Download, “Linux ARM (experimental)”
- `$ cd ~/Downloads`
- `$ tar Jxf arduino-1.6.*-linuxarm.tar.xz`
- `$ cd arduino-1.6.*-linuxarm`
- `$ ./install.sh`
- `$ ./install.sh`
- Start the Arduino IDE, set Board and Port
- Open the Blink example, compile and upload
- If using Nano, use built in LED on pin 13
- If not Nano, wire LED and resistor to a pin, change program to suit.



# ATtiny

- Attiny 45 is a tiny Arduino (6 I/O pins, 4kb memory)
- Use Arduino IDE to set up:
  - Open **File**→**Preferences**
  - Go to “Additional Boards Manager URL”
    - `https://raw.githubusercontent.com/damellis/attiny/ide-1.6.x-boards-manager/package\_damellis\_attiny\_index.json`
  - Click OK
  - Open **Tools**→**Board**→**Boards Manager**
  - Scroll to the bottom to “attiny”
  - Click once, Install button will appear, click it
  - Should see “INSTALLED” next to “attiny” when complete
  - Should now have two ATtiny options in **Tools**→**Board** menu:
    - ATtiny 25/45/85
    - ATtiny 24/44/84

# Set up Arduino as ATtiny programmer

- Load sketch `File`→`Examples`→`11.ArduinoISP`→`ArduinoISP`
- Upload to Arduino.
- Go to `Tools`→`Board` and select "ATtiny 25/45/85".
- Go to `Tools`→`Processor` and select "ATtiny 45".
- Go to `Tools`→`Clock` and select "Internal 1MHz".
- Go to `Tools`→`Programmer` and select "Arduino as ISP".



# Connect Attiny to Arduino, upload sketch


- Wire up ATtiny to Arduino with jumpers (see below).
- If Nano, put 47uF capacitor between RST (+) and GND (-).
- Wire an LED and resistor to pin 5 (logical pin 0).
- Load the Blink sketch from Examples (or from GitHub).
- Modify to use pin 0 instead of 13.
- Upload, LED blinks.

Pin name	Attiny pin	Nano	Uno
RST	1	D10	10
GND	4	GND	GND
MOSI	5	D11	11
MISO	6	D12	12
SCK	7	D13	13
VCC	8	5V	5V

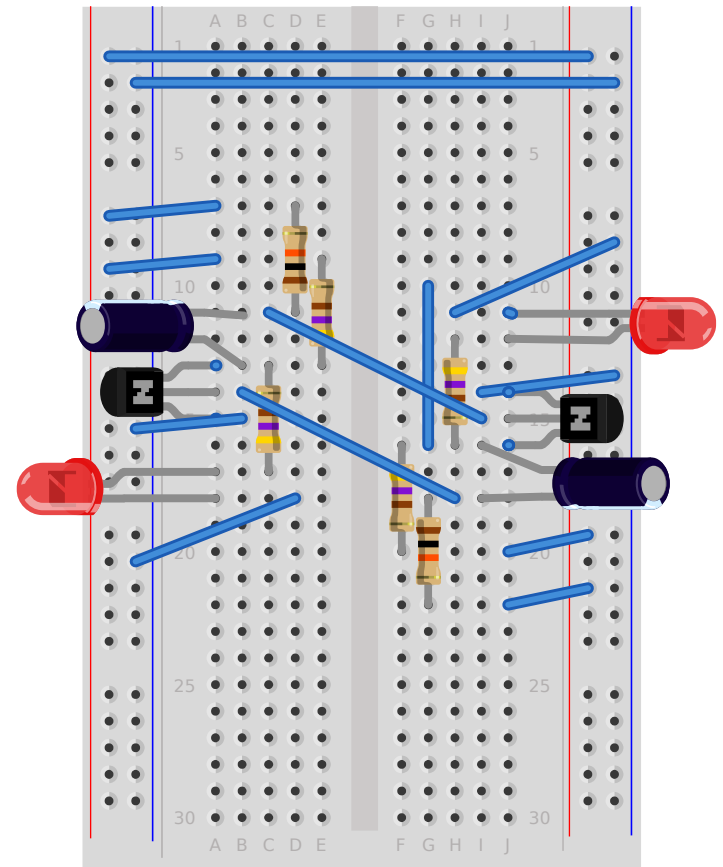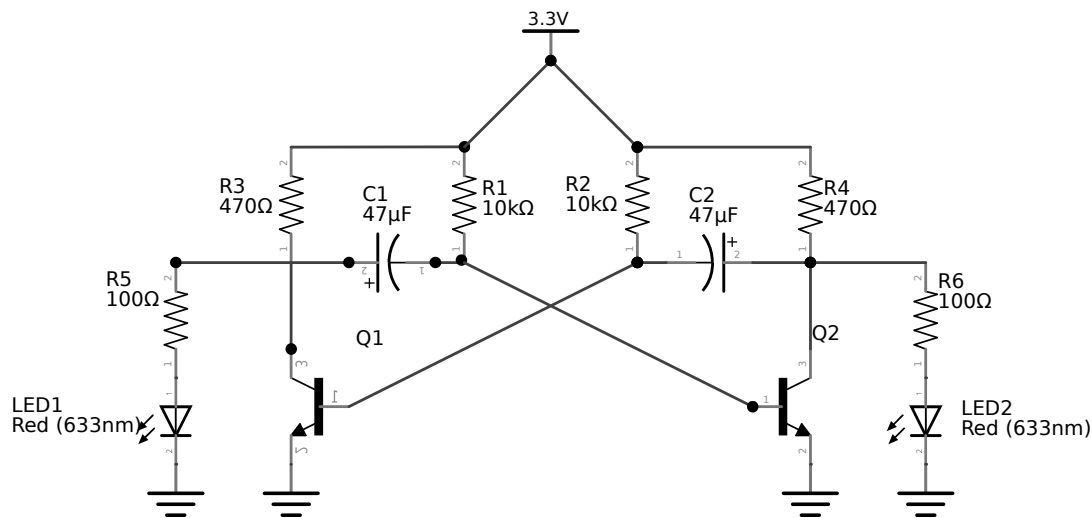
# Transistor Astable Multivibrator

- Similar to the 555 astable multivibrator but with super simple transistor
- Timing similar to 555:  $R1 \cdot C1$  and  $R2 \cdot C2$
- Note: transistors as switches – useful for Raspberry Pi pins, too



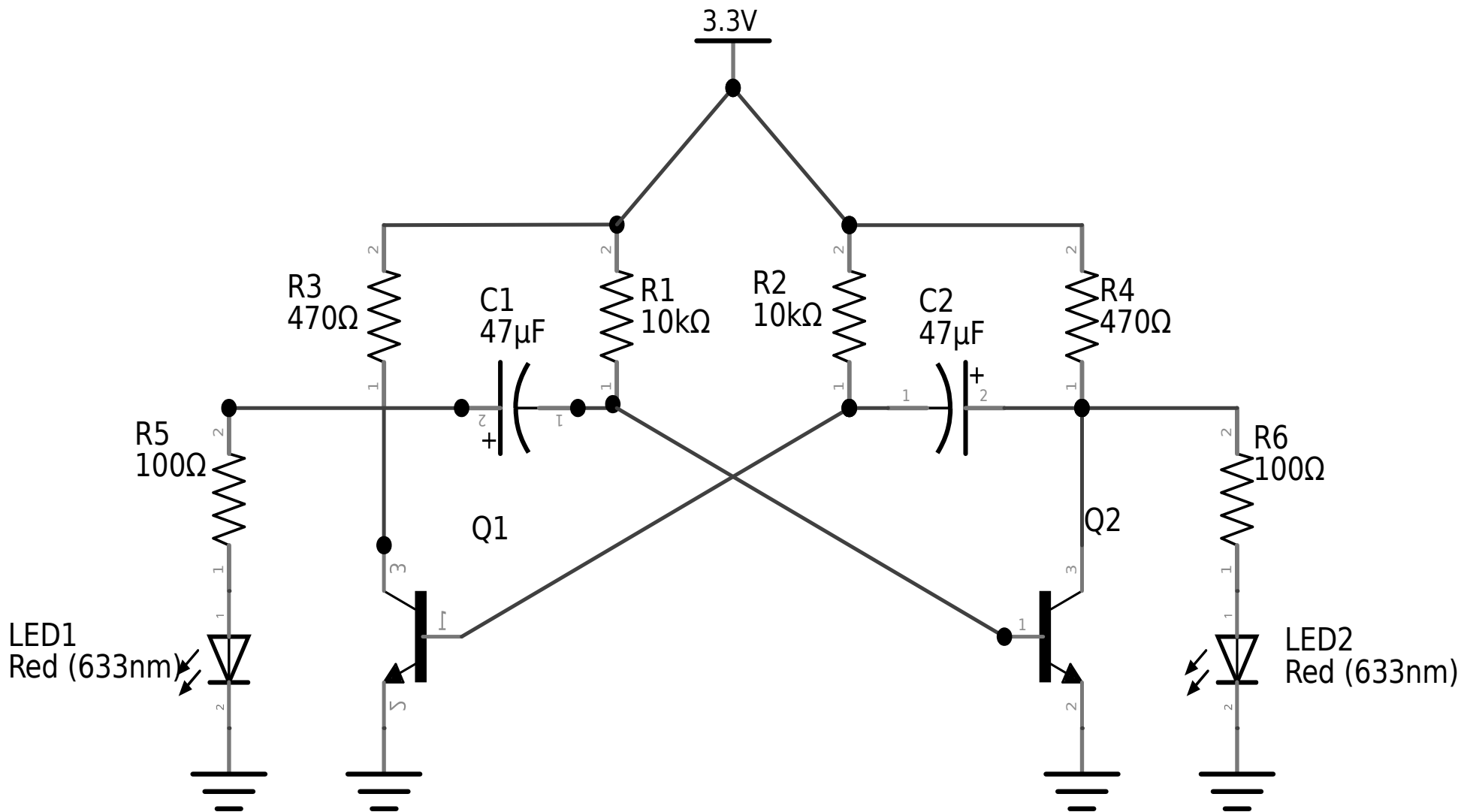


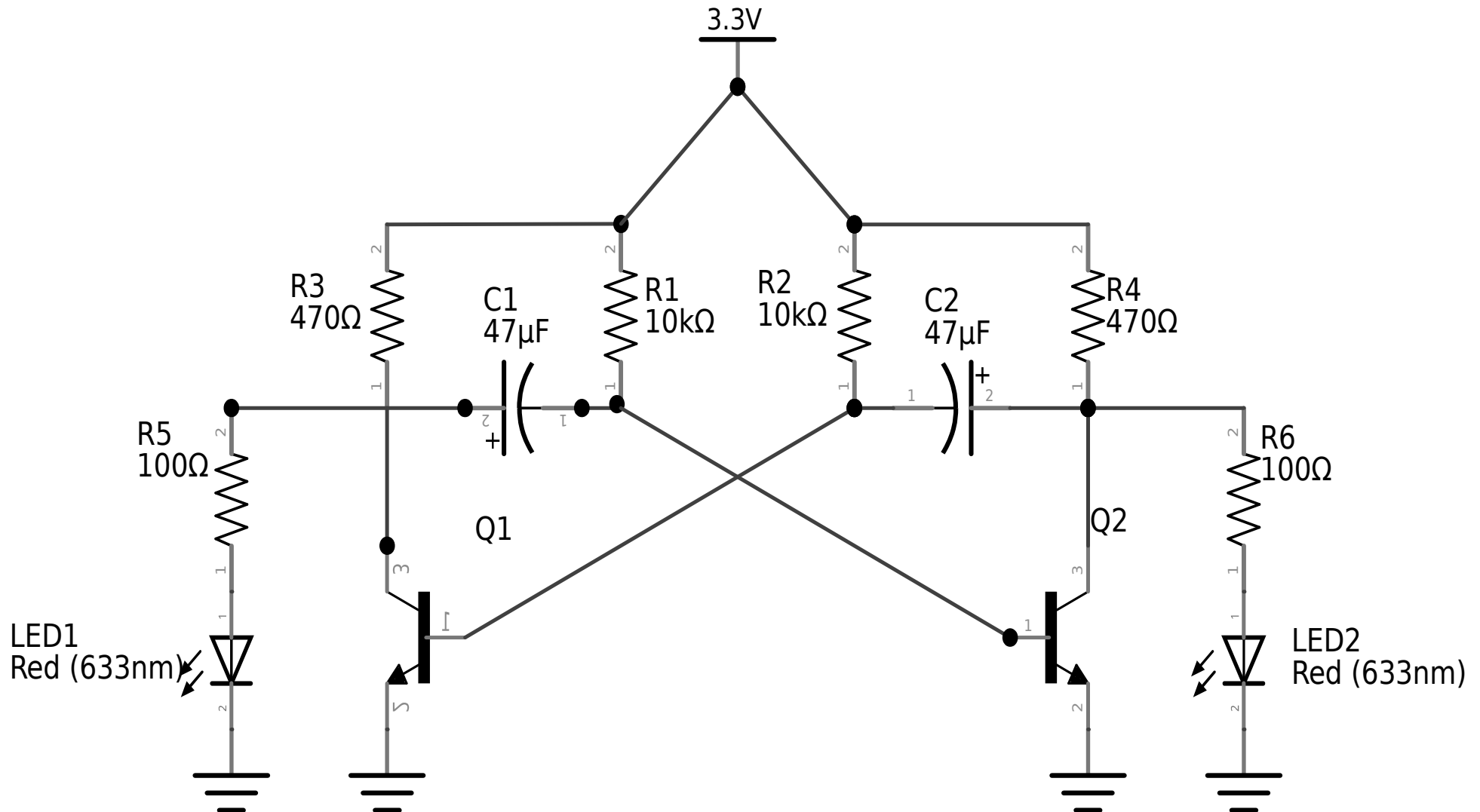- Transistors Q1 and Q2 are switches (rather than amplifiers)
- Timing determined by  $R1 \cdot C1$  and  $R2 \cdot C2$
- If C1 discharged, C2 charged, then Q1 on, Q2 off
- C1 charges until it turns on Q2
- Voltage on C2 drops, which turns off Q1


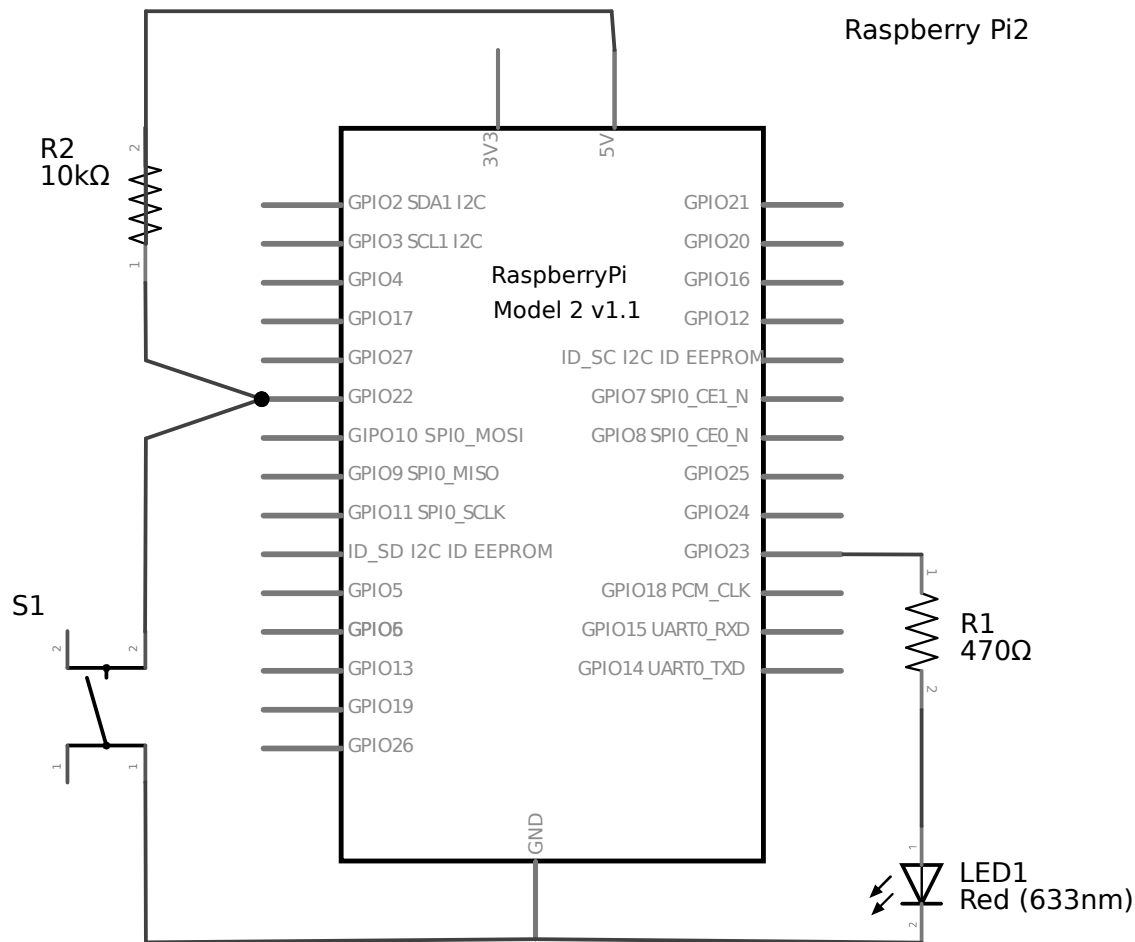
# Pi as Intermediary

- Pushbutton press turns LED on, release turns LED off



# RpiReadWrite.py (on GitHub)

```
import RPi.GPIO as GPIO
import time


BUTTON = 22
LED = 23

GPIO.setmode(GPIO.BCM)
GPIO.setup(BUTTON, GPIO.IN)
GPIO.setup(LED, GPIO.OUT)

try:
    while True:
        inputValue = GPIO.input(BUTTON)
        if (True == inputValue):
            GPIO.output(LED, GPIO.HIGH)
        else:
            GPIO.output(LED, GPIO.LOW)
        time.sleep(2)
except KeyboardInterrupt:
    GPIO.cleanup()
```



# Reference

 

## Raspberry Pi 3 GPIO Header

Pin#	NAME		NAME	Pin#
01	3.3v DC Power		DC Power 5v	02
03	GPIO02 (SDA1 , I <sup>2</sup> C)		DC Power 5v	04
05	GPIO03 (SCL1 , I <sup>2</sup> C)		Ground	06
07	GPIO04 (GPIO_GCLK)		(TXD0) GPIO14	08
09	Ground		(RXD0) GPIO15	10
11	GPIO17 (GPIO_GEN0)		(GPIO_GEN1) GPIO18	12
13	GPIO27 (GPIO_GEN2)		Ground	14
15	GPIO22 (GPIO_GEN3)		(GPIO_GEN4) GPIO23	16
17	3.3v DC Power		(GPIO_GEN5) GPIO24	18
19	GPIO10 (SPI_MOSI)		Ground	20
21	GPIO09 (SPI_MISO)		(GPIO_GEN6) GPIO25	22
23	GPIO11 (SPI_CLK)		(SPI_CE0_N) GPIO08	24
25	Ground		(SPI_CE1_N) GPIO07	26
27	ID_SD (I <sup>2</sup> C ID EEPROM)		(I <sup>2</sup> C ID EEPROM) ID_SC	28
29	GPIO05		Ground	30
31	GPIO06		GPIO12	32
33	GPIO13		Ground	34
35	GPIO19		GPIO16	36
37	GPIO26		GPIO20	38
39	Ground		GPIO21	40

Rev. 2  
29/02/2016

[www.element14.com/RaspberryPi](http://www.element14.com/RaspberryPi)

# Components

