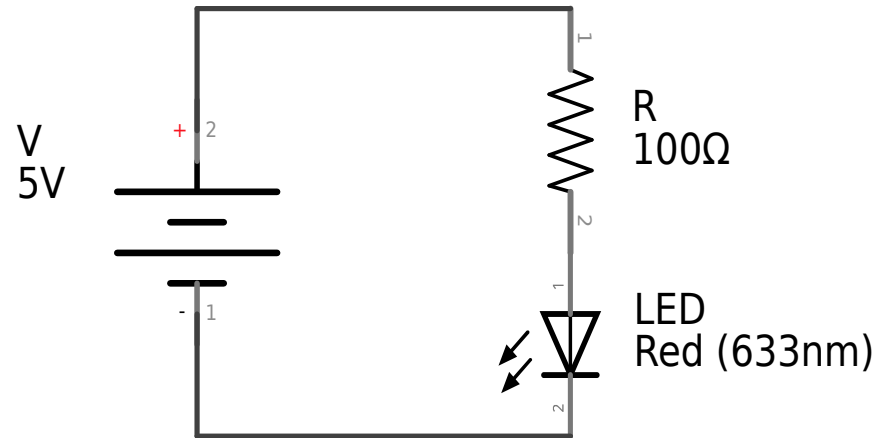


12 Ways to Blink an LED



Charlotte Hackerspace
Neil Roeth

LED basic circuit





- Need to limit current (no magic smoke)
- $V = V_{\text{LED}} + V_R$
- $V_R = IR$ (Ohm's Law)
- $V = V_{\text{LED}} + IR \Rightarrow R = (V - V_{\text{LED}})/I$
- LED: $V_{\text{LED}} \sim 2.5V$
- Raspberry Pi: 3.3V, 16mA
- $R = (3.3 - 2.5)/0.016 = 50 \text{ ohms}$
- Arduino: 5V, 40mA
- $R = (5 - 2.5)/0.040 = 62.5 \text{ ohms}$
- Bigger is safer

Blink LED with pushbutton

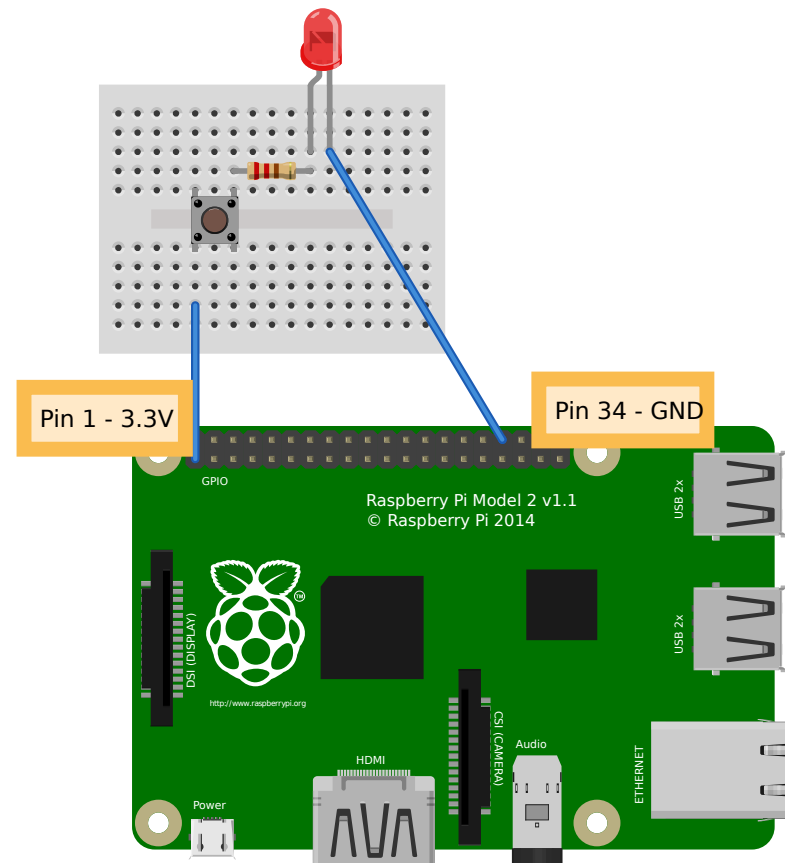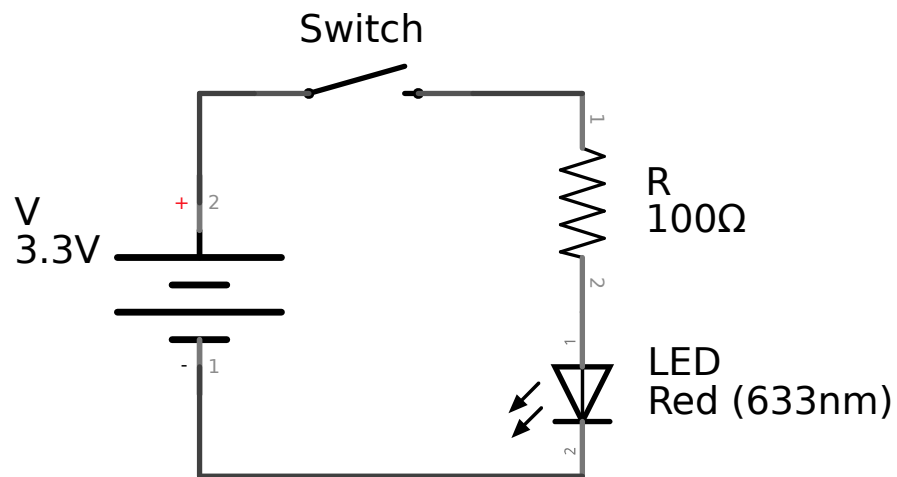

Blink LED with Pi

Raspberry Pi1

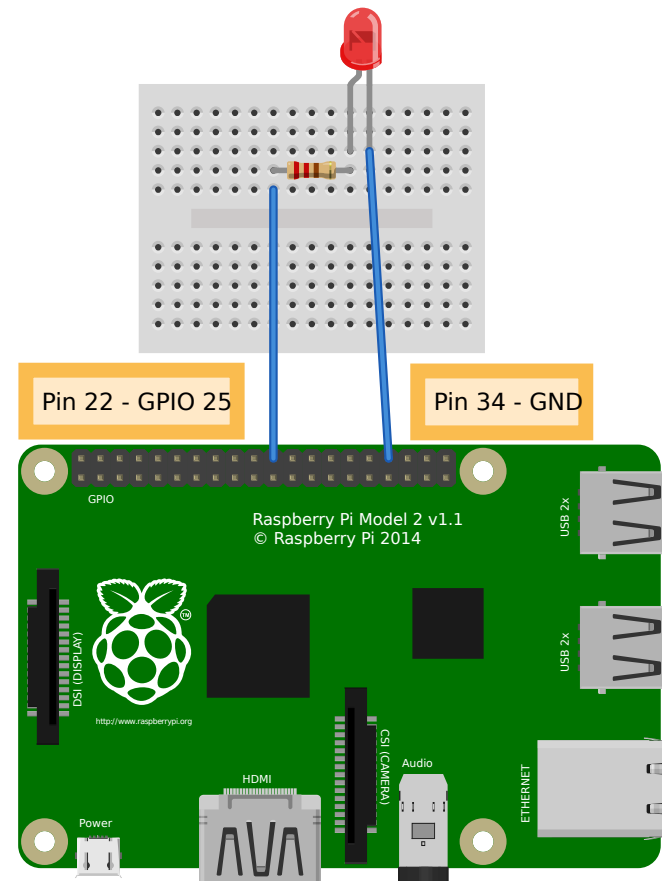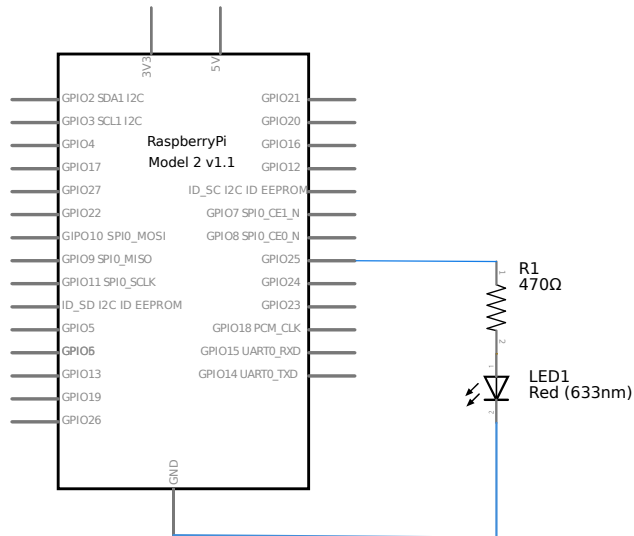

- Create a file named BlinkRaspberryPi.py with Python code:

```
import RPi.GPIO as GPIO
import time
```

```
GPIO.setmode(GPIO.BCM)
GPIO.setup(25, GPIO.OUT)
```



```
while True:
    GPIO.output(25, GPIO.HIGH)
    time.sleep(1)
    GPIO.output(25, GPIO.LOW)
    time.sleep(1)
```

- Ensure you have the Python libraries for accessing GPIO pins installed:

```
$ sudo apt-get install python-rpi.gpio python3-rpi.gpio
```


- Run it: `python BlinkRaspberryPi.py`
- What does script do?
- Raspberry Pi has digital outputs only (HIGH, LOW)

555 Astable Multivibrator

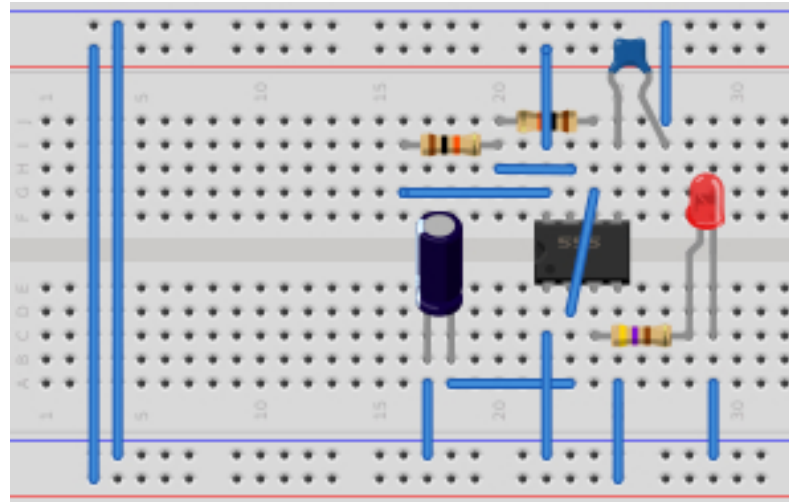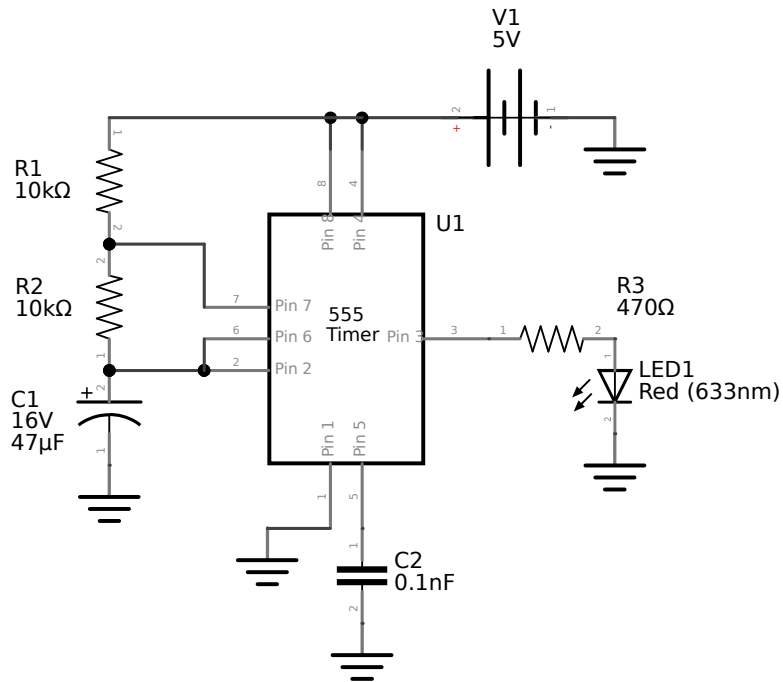


- Connect 5V from Pi to red rail, ground to blue rail
- Dot on IC is pin 1, C1 has +/-
- Timing is determined by how quickly capacitor C1 charges/discharges

How the 555 circuit works

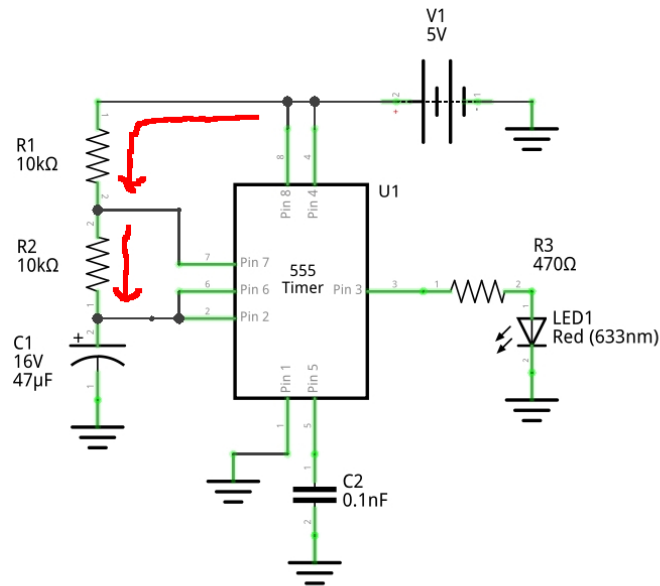

fritzing

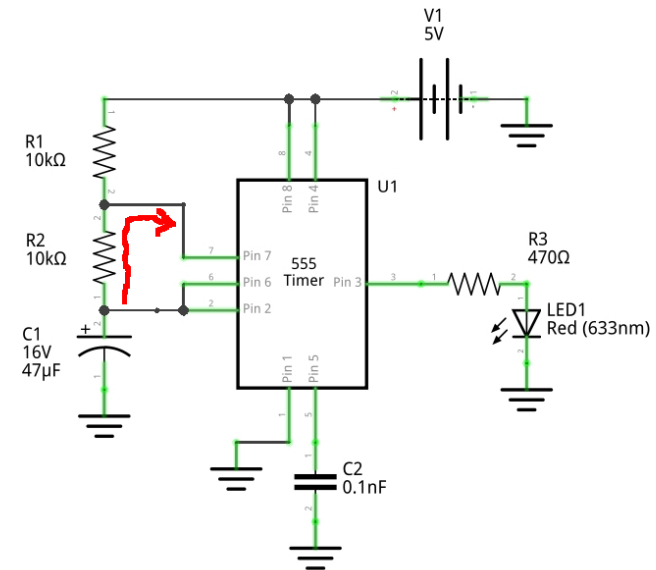

fritzing

- Charging (left): Capacitor C1 charges through R1 and R2
- When capacitor voltage reaches $\frac{2}{3} V_1$, pin 7 connects to ground
- Discharging (right): Capacitor C1 discharges through R2
- When capacitor drops to $\frac{1}{3} V_1$, pin 7 disconnects from ground
- Water analogy: voltage like pressure, current like flow rate
- Capacitor like bucket, resistor like hose restriction
- Bigger capacitor or bigger resistor means longer time
- Time constant for charging = $(R1+R2)*C1$
- Time constant for discharging = $R2*C1$

Arduino

- <https://www.arduino.cc/> , Download, “Linux ARM (experimental)”
- `$ cd ~/Downloads`
- `$ tar Jxf arduino-1.6.*-linuxarm.tar.xz`
- `$ cd arduino-1.6.*-linuxarm`
- `$./install.sh`
- `$./install.sh`
- Start the Arduino IDE, set Board and Port
- Open the Blink example, compile and upload
- If using Nano, use built in LED on pin 13
- If not Nano, wire LED and resistor to a pin, change program to suit.

ATtiny

- Attiny 45 is a tiny Arduino (6 I/O pins, 4kb memory)
- Use Arduino IDE to set up:
 - Open **File**→**Preferences**
 - Go to “Additional Boards Manager URL”
 - https://raw.githubusercontent.com/damellis/attiny/ide-1.6.x-boards-manager/package_damellis_attiny_index.json
 - Click OK
 - Open **Tools**→**Board**→**Boards Manager**
 - Scroll to the bottom to “attiny”
 - Click once, Install button will appear, click it
 - Should see “INSTALLED” next to “attiny” when complete
 - Should now have two ATtiny options in **Tools**→**Board** menu:
 - ATtiny 25/45/85
 - ATtiny 24/44/84

Set up Arduino as ATtiny programmer

- Load sketch `File`→`Examples`→`11.ArduinoISP`→`ArduinoISP`
- Upload to Arduino.
- Go to `Tools`→`Board` and select "ATtiny 25/45/85".
- Go to `Tools`→`Processor` and select "ATtiny 45".
- Go to `Tools`→`Clock` and select "Internal 1MHz".
- Go to `Tools`→`Programmer` and select "Arduino as ISP".



Connect Attiny to Arduino, upload sketch


- Wire up ATtiny to Arduino with jumpers (see below).
- If Nano, put 47uF capacitor between RST (+) and GND (-).
- Wire an LED and resistor to pin 5 (logical pin 0).
- Load the Blink sketch from Examples (or from GitHub).
- Modify to use pin 0 instead of 13.
- Upload, LED blinks.


| Pin name | Attiny pin | Nano | Uno |
|----------|------------|------|-----|
| RST | 1 | D10 | 10 |
| GND | 4 | GND | GND |
| MOSI | 5 | D11 | 11 |
| MISO | 6 | D12 | 12 |
| SCK | 7 | D13 | 13 |
| VCC | 8 | 5V | 5V |

Transistor Astable Multivibrator

 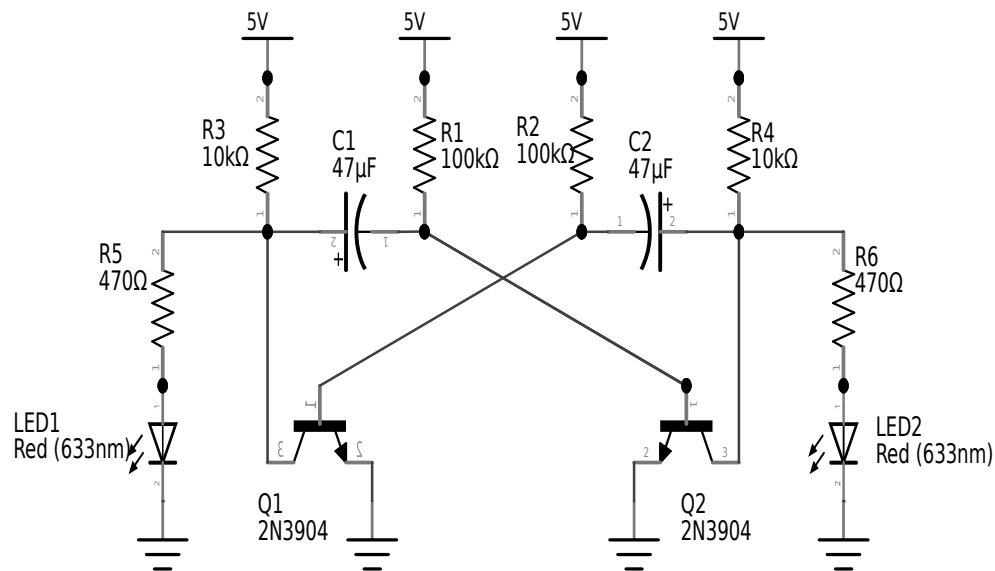- Similar to the 555 astable multivibrator but with super simple transistor
- Timing similar to 555: $R1 \cdot C1$ and $R2 \cdot C2$
- Note: transistors as switches – useful for Raspberry Pi pins, too




 

 


How It Works (briefly)

 - Transistors Q1 and Q2 are switches (rather than amplifiers)
- Timing determined by $R1 \cdot C1$ and $R2 \cdot C2$
- If C1 discharged, C2 charged, then Q1 on, Q2 off
- C1 charges until it turns on Q2
- Voltage on C2 drops, which turns off Q1



Pi as Intermediary

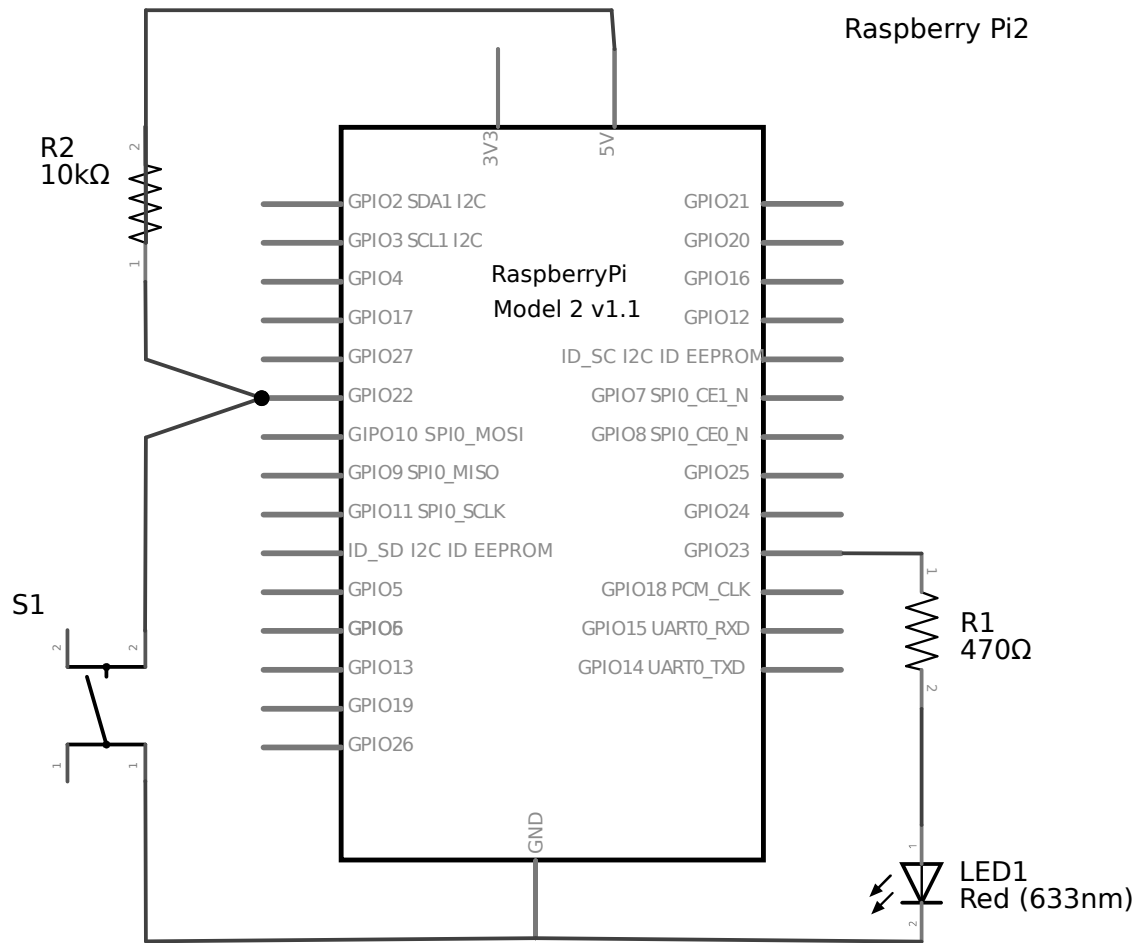- Pushbutton press turns LED on, release turns LED off



RpiReadWrite.py (on GitHub)


```
import RPi.GPIO as GPIO
import time

BUTTON = 22
LED = 23

GPIO.setmode(GPIO.BCM)
GPIO.setup(BUTTON, GPIO.IN)
GPIO.setup(LED, GPIO.OUT)

try:
    while True:
        inputValue = GPIO.input(BUTTON)
        if (GPIO.LOW == inputValue):
            GPIO.output(LED, GPIO.HIGH)
        else:
            GPIO.output(LED, GPIO.LOW)
        time.sleep(2)
except KeyboardInterrupt:
    GPIO.cleanup()
```

Reference

 

Raspberry Pi 3 GPIO Header

| Pin# | NAME | NAME | Pin# |
|------|------------------------------------|------------------------------------|------|
| 01 | 3.3v DC Power | DC Power 5v | 02 |
| 03 | GPIO02 (SDA1 , I ² C) | DC Power 5v | 04 |
| 05 | GPIO03 (SCL1 , I ² C) | Ground | 06 |
| 07 | GPIO04 (GPIO_GCLK) | (TXD0) GPIO14 | 08 |
| 09 | Ground | (RXD0) GPIO15 | 10 |
| 11 | GPIO17 (GPIO_GEN0) | (GPIO_GEN1) GPIO18 | 12 |
| 13 | GPIO27 (GPIO_GEN2) | Ground | 14 |
| 15 | GPIO22 (GPIO_GEN3) | (GPIO_GEN4) GPIO23 | 16 |
| 17 | 3.3v DC Power | (GPIO_GEN5) GPIO24 | 18 |
| 19 | GPIO10 (SPI_MOSI) | Ground | 20 |
| 21 | GPIO09 (SPI_MISO) | (GPIO_GEN6) GPIO25 | 22 |
| 23 | GPIO11 (SPI_CLK) | (SPI_CE0_N) GPIO08 | 24 |
| 25 | Ground | (SPI_CE1_N) GPIO07 | 26 |
| 27 | ID_SD (I ² C ID EEPROM) | (I ² C ID EEPROM) ID_SC | 28 |
| 29 | GPIO05 | Ground | 30 |
| 31 | GPIO06 | GPIO12 | 32 |
| 33 | GPIO13 | Ground | 34 |
| 35 | GPIO19 | GPIO16 | 36 |
| 37 | GPIO26 | GPIO20 | 38 |
| 39 | Ground | GPIO21 | 40 |

Rev. 2
29/02/2016

www.element14.com/RaspberryPi

Components

